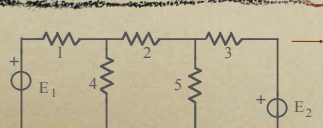


Esercitazione 4

Esercizi: sovrapposizione degli effetti



$$I_3 = 2,14 \text{ A.}$$

- $R_1 = 4,5 \Omega;$
- $R_2 = 10 \Omega;$
- $R_3 = 15 \Omega;$
- $R_4 = 35 \Omega;$
- $R_5 = 200 \Omega;$
- $E_1 = 290 \text{ V};$
- $E_2 = 180 \text{ V}.$

Es. 6.0

Esercizi.

