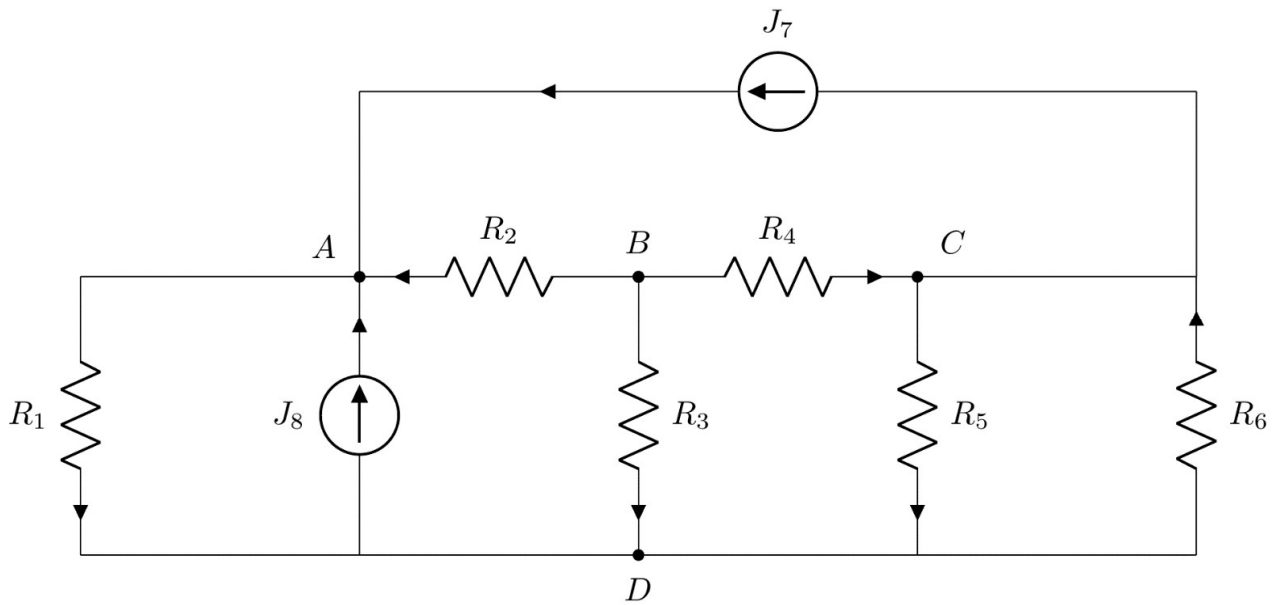


Risolvere il seguente circuito (si veda l'Esercizio#2 fatto in Matlab).



$$R_1 = 1 \, \Omega, R_2 = 2 \, \Omega, R_3 = 3 \, \Omega, R_4 = 4 \, \Omega$$

$$R_5 = 5 \, \Omega, R_6 = 6 \, \Omega, J_7 = 7 \, A, J_8 = 8 \, A$$

